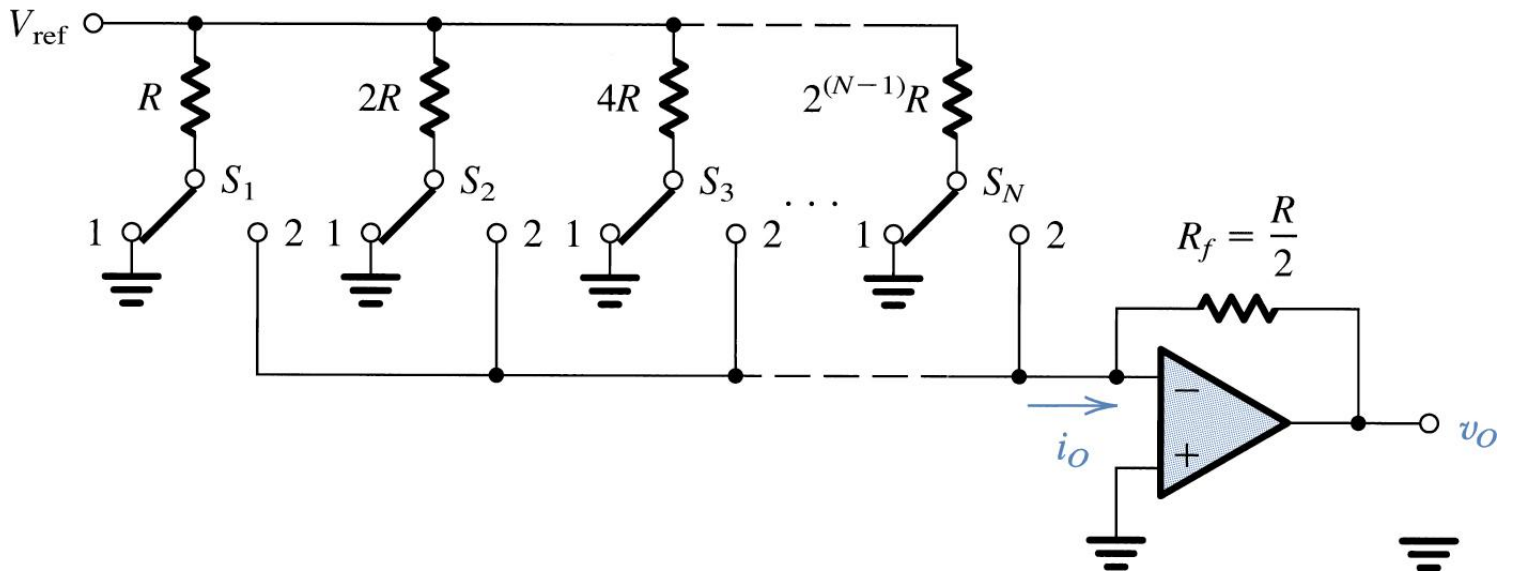


1) Basic circuit using binary-weighted resistor.
 N binary-weighted resistors $R, 2R, 2^2R, \dots, 2^{N-1}R$



An N -bit D/A converter using a binary-weighted resistive ladder network.

N -bit digital input $D: b_1b_2b_3\dots b_N$

Rewritten in decimal $D = \frac{b_1}{2^1} + \frac{b_2}{2^2} + \frac{b_3}{2^3} \dots + \frac{b_N}{2^N}$


Where b_i is the switch S_i , $b_i=0$, when switch is connecting to 1
 $b_i=1$, when switch is connecting to 2

$$\begin{aligned} i_o &= \frac{V_{ref}}{R} b_1 + \frac{V_{ref}}{2R} b_2 + \frac{V_{ref}}{2^2R} b_3 \dots + \frac{V_{ref}}{2^{N-1}R} b_N \\ &= \frac{V_{ref}}{2R} \left(\frac{b_1}{2^1} + \frac{b_2}{2^2} + \frac{b_3}{2^3} \dots + \frac{b_N}{2^N} \right) \\ &= \frac{V_{ref}}{2R} D \end{aligned}$$

$$V_o = -i_o R_f = -\frac{V_{ref}}{2R} D * R/2 = -V_{ref} D$$

Remarks: N increase, spread between R and $2^{N-1}R$ increases
 Difficult to maintain accuracy in resistor value

2) Improved R-2R ladders

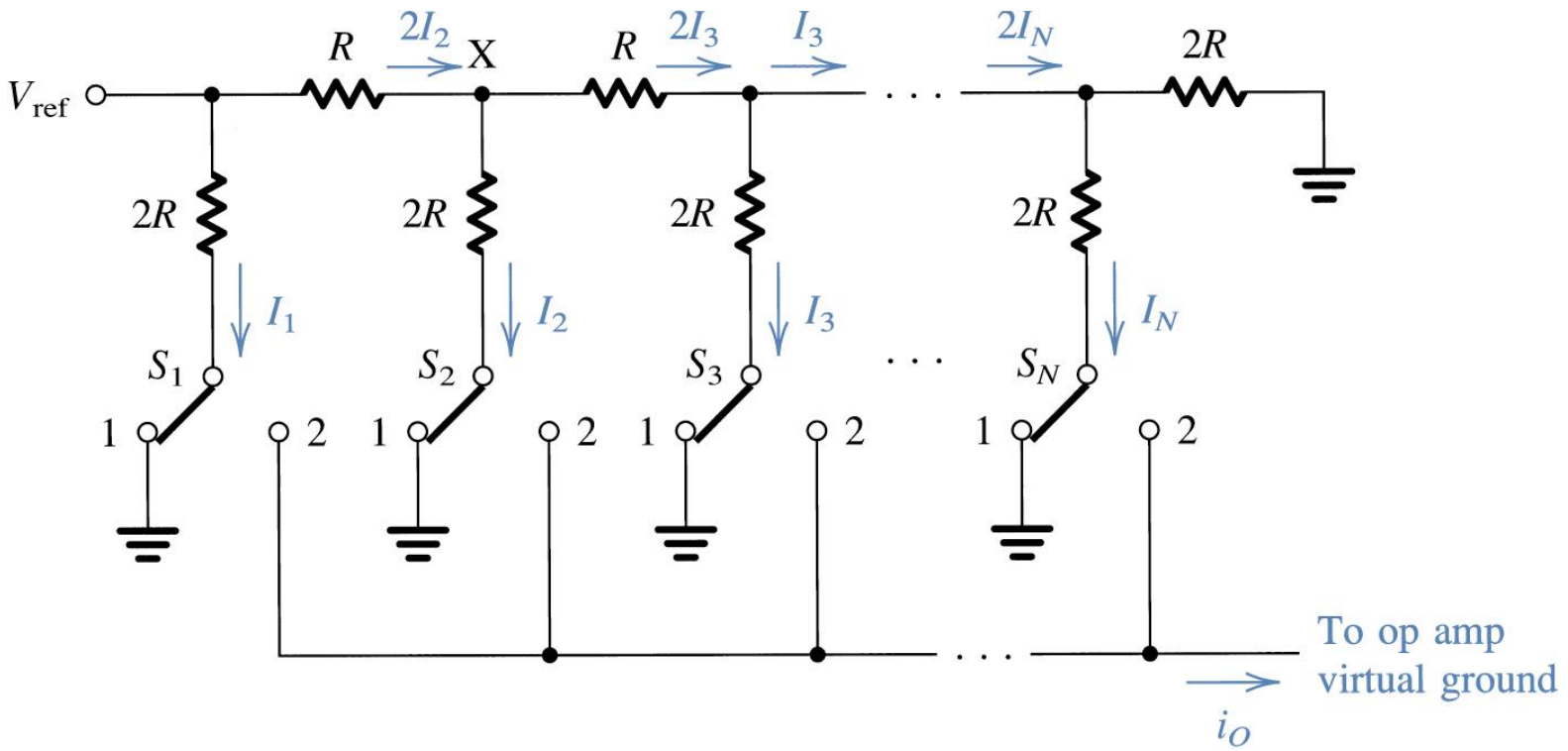


Basic circuit configurations of a DAC utilizing an R - $2R$ ladder network.

$$I_1 = 2I_2 = 4I_3 = \dots = 2^{n-1}I_N$$

$$i_o = \frac{V_{\text{ref}}}{R} D$$

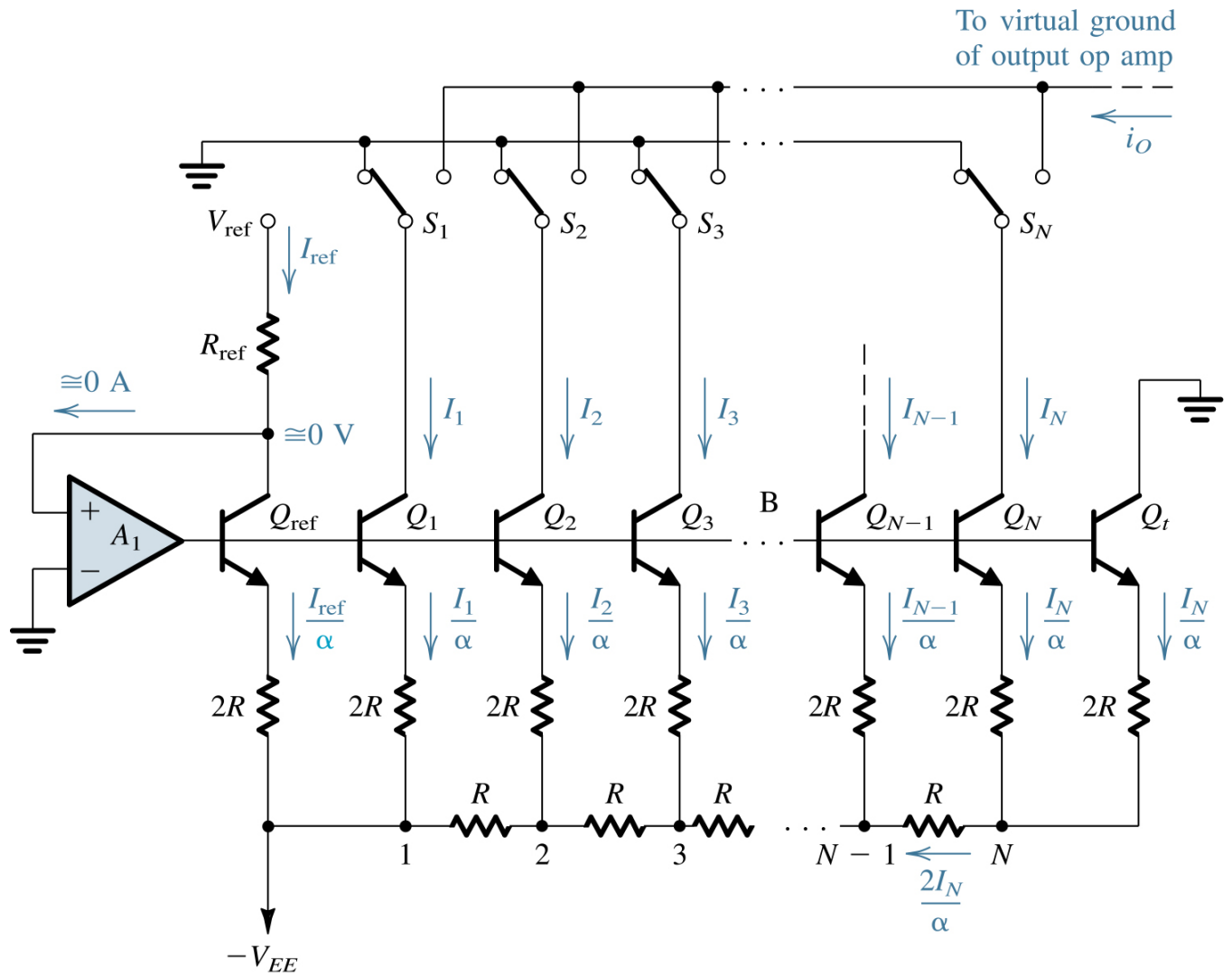3) A practical implementation of R-2R ladders



A practical circuit implementation of a DAC utilizing an R-2R ladder network.